PAPER ID-311408

Subject Code: BEC302

Roll No: | | | | | | | | | | | | | |

BTECH
(SEM III) THEORY EXAMINATION 2023-24
DIGITAL SYSTEM DESIGN

TIME: 3HRS **M.MARKS: 70**

Note: 1. Attempt all Sections. If require any missing data; then choose suitably.

SECTION A

1. Attempt *all* questions in brief. 2 x 7 = 14

Q no.	Question	Marks
a.	What is the purpose of binary arithmetic in digital logic design?	2
b.	Explain the concept of signed magnitude representation.	2
c.	Explain the operation of a multiplexer.	2
d.	How does a full adder differ from a half adder?	2
e.	What are the basic building blocks of sequential logic circuits?	2
f.	What is fan-out in logic families?	2
g.	What are the key specifications of a DAC?	2

SECTION B

2. Attempt any *three* of the following: 7 x 3 = 21

a.	Convert the following. Hexadecimal equivalent of the decimal number 256 Decimal equivalent of $(123)_9$ 378.93_{10} to octal Convert A3BH and 2F3H into binary.	7
b.	Design a full adder by constructing the truth table and simplify the output equations.	7
c.	Describe the operation of various flip-flops, including S-R, JK, D, and T flip-flops	7
d.	Draw a circuit diagram of a CMOS inverter. Draw its transfer characteristics and explain its operation.	7
e.	Explain switched capacitor and give its applications	7

SECTION C

3. Attempt any *one* part of the following: 7 x 1 = 7

a.	Use Karnaugh maps to simplify the Boolean function: F(A, B,C,D) = Σ(1, 2, 4, 6, 9, 10, 11, 12, 13, 14, 15).	7
b.	State and Prove Demorgan's theorem.	7

4. Attempt any *one* part of the following: 7 x 1 = 7

a.	Implement a full adder using NAND gates.	7
b.	Design 2-bit magnitude comparator.	7

5. Attempt any *one* part of the following: 7 x 1 = 7

a.	Compare and contrast Mealy and Moore machines and discuss their applications in digital systems design.	7
b.	Explain positive edge triggered D-flip-flop with the help of circuit diagram and waveforms.	7

6. Attempt any *one* part of the following: 7 x 1 = 7

a.	Explain the characteristics and specifications of TTL NAND gates, including noise margin, propagation delay, fan-in, and fan-out.	7
b.	Describe the concept of programmable logic devices (PLDs) and explain how they are used for logic implementation in digital systems.	7

7. Attempt any *one* part of the following: 7 x 1 = 7

a.	Explain the principle of operation of an R2R ladder DAC.	7
b.	Describe the principle of operation of a successive approximation ADC.	7

QP24DP2_290 | 16-03-2024 13:26:58 | 117.55.242.132